
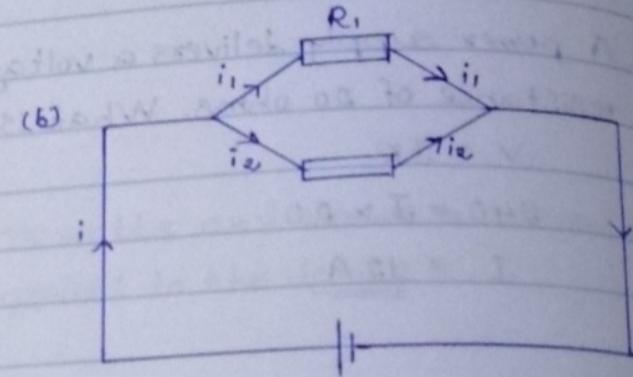


Tutorial 07

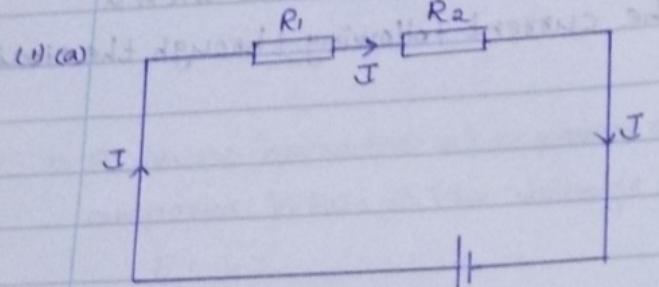

If $R_1 = 6\Omega$, $R_2 = 12\Omega$, $I = 1A$, find equivalent resistance and V .

$$(a) \text{ Total Resistance} = R_1 + R_2 = 18\Omega$$

$$I = 1A$$

$$V = ?$$

$$V = IR$$

$$= 1 \times 18$$

$$= \underline{\underline{18V}}$$

$$(b) \text{ Total Resistance} = \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{6} + \frac{1}{12} = \frac{3}{12} = \frac{1}{4}$$

$$\frac{1}{R_T} = \frac{1}{6} + \frac{1}{12} = \frac{3}{12} = \frac{1}{4}$$

$$R_T = 4\Omega$$

$$V = IR$$

$$I = 1A$$


$$= 1 \times 4$$

$$= 4V$$

$$= \underline{\underline{4V}}$$

(2) Three resistors 6Ω , 12Ω and 4Ω are connected in series to an electronic supply of $12V$.

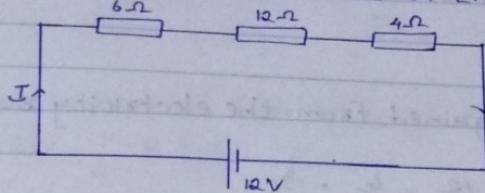(i) Calculate the total resistance of these three resistors.



$$R_T = 6\Omega + 12\Omega + 4\Omega = \underline{\underline{22\Omega}}$$

(ii) What is the current gain from the electric supply?


$$V = JR$$

$$J = \frac{V}{R}$$

$$= \frac{12}{22}$$

$$= \underline{\underline{0.55A}}$$

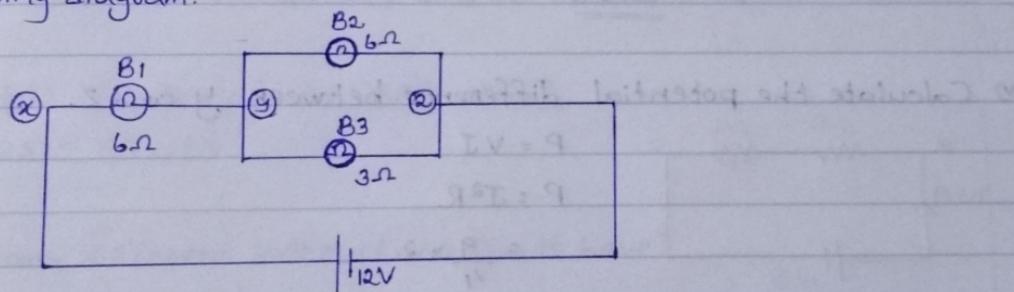(3) Three bulbs, B_1 , B_2 , B_3 are connected to $12V$ supply as shown in the following diagram.




(i) Calculate the total resistance of the two bulbs B_2 and B_3 (between y and z).

B_2 and B_3 are parallelly connected to each other.

$$\therefore \frac{1}{R_T} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6} + \frac{1}{3} = \frac{3}{6} = \frac{1}{2}$$

$$R_T = \underline{\underline{2\Omega}}$$

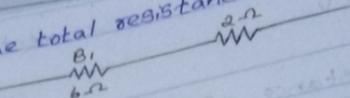(ii) What is the total resistance between the two points x and z



$$RT' = (6 + 2)\Omega$$

$$RT' = \underline{8\Omega}$$

(iii) What is the current gained from the electricity supply?

$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{8} = \frac{6}{4} = \frac{3}{2}$$

$$I = \underline{1.5A}$$

(iv) Calculate the potential difference between x and y.

$$P = VI$$

$$P = I^2 R$$

$$P = (1.5)^2 \times 6$$


$$P = \left(\frac{3}{2}\right)^2 \times 6$$

$$P = \frac{9 \times 6}{4}$$

$$P = \frac{27}{2}$$

$$P = \underline{13.5W}$$

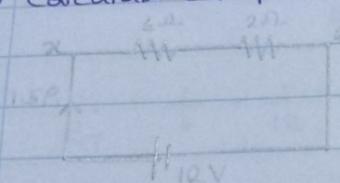(v) Calculate the potential difference between y and z.



$$P = VI$$

$$P = I^2 R$$


$$= \frac{9}{4} \times 2$$

$$P = \underline{4.5W}$$

SAD

WEB

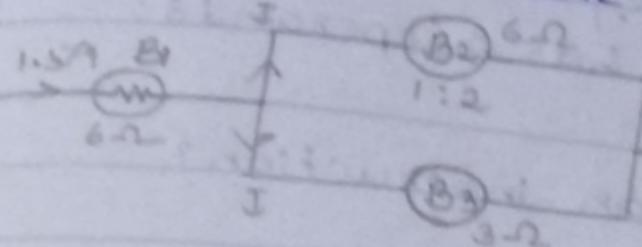(vi) Calculate the current flow through B_2 .



$$J_{B_2} = \frac{1.5 \times 1}{3} = \frac{1}{2}$$


$$J_{B_2} = \underline{0.5\text{A}}$$

(vii) Calculate the current flow through B_3 .

$$\frac{1.5 \times 2}{3} = \frac{1 \times 2}{2} = 1\text{A}$$

$$J_{B_3} = \underline{1\text{A}}$$

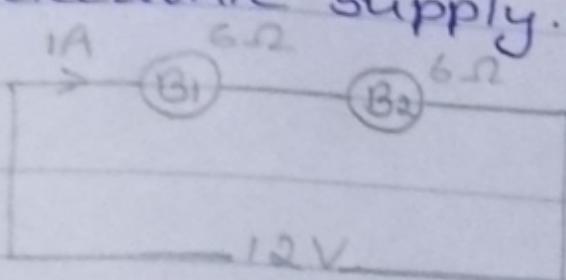(viii) If B_3 is removed, then what would be the current gain from the electronic supply.



$$J = \frac{V}{R} = \frac{12}{12}$$

$$J = \underline{1\text{A}}$$